

Boolean Algebra & Logic Gates

Classwork Problems with Solutions

Week 2 · Summer 2026 · Mansur Mulk, PhD.

§1 Postulates & Theorems

§2 Boolean Functions & Truth Tables

§3 De Morgan & Complement

§4 Algebraic Simplification

§5 Minterms, Maxterms & Canonical Forms

§6 Standard Forms & Gate Implementation

Section 1

Postulates & Theorems

Apply Huntington's postulates to prove Boolean identities

CW 1 — Prove the Boolean Identities

Use Huntington Postulates (P1–P6) and Theorems (T1–T8)

Mansur Mulk

Prove each of the following using only the postulates and theorems of Boolean algebra. State the law used at each step.

(a)

Prove:

$$x + xy = x$$

Hint: Use absorption / idempotency / distribution

(d)

Prove:

$$(x + y)(x + y') = x$$

Hint: Use absorption / idempotency / distribution

(b)

Prove:

$$x(x + y) = x$$

Hint: Use absorption / idempotency / distribution

(e)

Prove:

$$xy + xy' = x$$

Hint: Use absorption / idempotency / distribution

(c)

Prove:

$$x + x'y = x + y$$

Hint: Use absorption / idempotency / distribution

(f)

Prove:

$$x'y + xy' + xy = x + y$$

Hint: Use absorption / idempotency / distribution

CW 1 — Solutions: Prove Boolean Identities

Each step cites the postulate or theorem used

(a) $x + xy$

$= x \cdot 1 + xy$ [P2b]
 $= x(1+y)$ [P5a]
 $= x \cdot 1$ [T2a]
 $= x$ [P2b] ✓

(b) $x(x + y)$

$= xx + xy$ [P5a]
 $= x + xy$ [T1b]
 $= x$ [T6a Absorption] ✓

(c) $x + x'y$

$= (x+x')(x+y)$ [P5b distributive]
 $= 1 \cdot (x+y)$ [P6a]
 $= x+y$ [P2b] ✓

(d) $(x+y)(x+y')$

$= x + yy'$ [P5b]
 $= x + 0$ [P6b]
 $= x$ [P2a] ✓

(e) $xy + xy'$

$= x(y+y')$ [P5a]
 $= x \cdot 1$ [P6a]
 $= x$ [P2b] ✓

(f) $x'y + xy' + xy$

$= x'y + x(y'+y)$ [P5a]
 $= x'y + x \cdot 1$ [P6a]
 $= x'y + x$ [P2b]
 $= x + y$ [T5a: $x+x'y=x+y$] ✓

Section 2

Boolean Functions & Truth Tables

Evaluate functions, build truth tables, identify gate diagrams

CW 2 — Truth Table & Gate Diagram: $F_1 = x + yz'$

Section 2: Boolean Functions

Mansur Mulk

(a) Complete the truth table for $F_1 = x + yz'$. (b) Draw the minimal two-level AND-OR gate diagram. (c) Identify the minterms where $F_1 = 1$.

x	y	z	yz'	$F_1=x+yz'$	Minterm
0	0	0	0	0	—
0	0	1	0	0	—
0	1	0	1	1	$m_2 = x'yz'$
0	1	1	0	0	—
1	0	0	0	1	$m_4 = xy'z'$
1	0	1	0	1	$m_5 = xy'z$
1	1	0	1	1	$m_6 = xyz'$
1	1	1	0	1	$m_7 = xyz$

Gate Diagram — $F_1 = x + yz'$

Inputs: x, y, z

Level 1 (NOT): $z \rightarrow \text{NOT} \rightarrow z'$

Level 1 (AND): $y, z' \rightarrow \text{AND} \rightarrow yz'$

Level 2 (OR): $x, yz' \rightarrow \text{OR} \rightarrow F_1$

Gate count: 1 NOT + 1 AND + 1 OR = 3 gates

Gate delays: 2 levels (AND→OR)

$F_1 = 1$ for minterms: {2, 4, 5, 6, 7}

$F_1(x,y,z) = \Sigma m(2, 4, 5, 6, 7)$

CW 3 — Simplify & Implement: $F_2 = x'y'z + x'yz + xy'$

Section 2: Equivalent Logic / Algebraic Manipulation

(a) Simplify F_2 to a minimal SOP. (b) Draw both the original and simplified gate diagrams. (c) State how many gates are saved.

Original expression (3 terms, 8 literals):

$$F_2 = x'y'z + x'yz + xy'$$

✓ Solution — Step-by-Step

Step 1 — Factor out $x'z$ from first two terms:

$$x'y'z + x'yz = x'z(y' + y) = x'z \cdot 1 = x'z$$

Step 2 — Write simplified form:

$$F_2 = x'z + xy'$$

Result: 2 terms, 4 literals (saves 4 literals!)

Gate comparison:

Original: 3 AND (3-input) + 1 OR (3-input) + 3 NOT = 7 gates

Simplified: 2 AND (2-input) + 1 OR + 2 NOT = 5 gates

Savings: 2 gates, 4 fewer literals

Gate Diagrams (Fig. 2.2)

(a) Original — $F_2 = x'y'z + x'yz + xy'$:

$$\text{NOT}(x) \rightarrow x' \quad \text{NOT}(y) \rightarrow y'$$

$$\text{AND}(x', y', z) \rightarrow x'y'z$$

$$\text{AND}(x', y, z) \rightarrow x'yz$$

$$\text{AND}(x, y') \rightarrow xy'$$

$$\text{OR}(x'y'z, x'yz, xy') \rightarrow F_2$$

$$= 3 \text{ AND} + 1 \text{ OR} + 2 \text{ NOT} \quad (3 \text{ levels if NOTs counted})$$

(b) Simplified — $F_2 = x'z + xy'$:

$$\text{NOT}(x) \rightarrow x' \quad \text{NOT}(y) \rightarrow y'$$

$$\text{AND}(x', z) \rightarrow x'z$$

$$\text{AND}(x, y') \rightarrow xy'$$

$$\text{OR}(x'z, xy') \rightarrow F_2$$

$$= 2 \text{ AND} + 1 \text{ OR} + 2 \text{ NOT} \quad (\text{TRUE 2-level SOP})$$

Section 3

De Morgan's Theorem & Complements

Find function complements; verify with truth tables

CW 4 — Find the Complement of Each Function

Section 3: De Morgan's Theorem

Mansur Mulk

Apply De Morgan's theorems repeatedly to find F' for each function. Simplify your result to a minimal form.

1

Find F_1'

$$F_1 = x'yz' + x'y'z$$

Recall: $(A+B)' = A'B'$ and $(AB)' = A'+B'$

2

Find F_2'

$$F_2 = x(y'z' + yz)$$

Recall: $(A+B)' = A'B'$ and $(AB)' = A'+B'$

3

Find F_3' — two methods

$$F_3 = (A+B)(A'+C)$$

Recall: $(A+B)' = A'B'$ and $(AB)' = A'+B'$

4

Apply Consensus theorem first

$$F_4 = AB + A'CD + BCD$$

Recall: $(A+B)' = A'B'$ and $(AB)' = A'+B'$

CW 4 — Solutions: Function Complements

De Morgan applied step-by-step

1

$$\begin{aligned}F_1' &= (x'yz' + x'y'z)' = (x'yz')' \cdot (x'y'z)' \\ &= (x+y'+z)(x+y+z')\end{aligned}$$

Note: (Sum of products $\rightarrow$ product of sums via dual DeMorgan)

2

$$\begin{aligned}F_2' &= [x(y'z' + yz)]' = x' + (y'z' + yz)' \\ &= x' + (y'z')' \cdot (yz)' \\ &= x' + (y+z)(y'+z')\end{aligned}$$

Note: (Distribute outer: $x' +$ inner complement)

Method 1 (DeMorgan directly):

$$\begin{aligned}F_3' &= [(A+B)(A'+C)]' = (A+B)' + (A'+C)' \\ &= A'B' + A(C') \\ F_3' &= A'B' + AC'\end{aligned}$$

Method 2 (Dual + complement literals):

$$\begin{aligned}\text{Dual of } F_3 &= (AB) + (A'C) \\ \text{Complement literals: } (A'B') + (AC') &= F_3' \quad \checkmark\end{aligned}$$

Note: (Both methods yield the same result)

4

First apply Consensus T9: BCD is consensus of AB & A'CD

$$F_4 = AB + A'CD \quad (\text{BCD removed})$$

Now find complement:

$$\begin{aligned}F_4' &= (AB + A'CD)' = (AB)' \cdot (A'CD)' \\ &= (A'+B') \cdot (A+C'+D')\end{aligned}$$

Note: (Simplify first using Consensus, then complement)

Section 4

Algebraic Simplification

Apply theorems to minimize literals and gate count

CW 5 — Simplify to Minimum Literals (Example 2.1)

Section 4: Algebraic Manipulation

Mansur Mulk

Simplify each expression to the minimum number of literals. Cite the theorem used at each step.

1

Simplify:

$$x(x' + y)$$

2

Simplify:

$$x + x'y$$

3

Simplify:

$$(x + y)(x + y')$$

4

Simplify:

$$xy + x'z + yz$$

5

Simplify:

$$AB + A'C + BC$$

6

Simplify:

$$(x + y)(x' + z)(y + z)$$

CW 5 — Solutions: Simplify to Minimum Literals

Mano Example 2.1 — all 5 results plus Consensus

Mansur Mulk

1

$$x(x' + y)$$

$$\begin{aligned} &= xx' + xy \text{ [P5a]} \\ &= 0 + xy \text{ [P6b]} \\ &= xy \text{ [P2a]} \end{aligned}$$

2

$$x + x'y$$

$$\begin{aligned} &= (x+x')(x+y) \text{ [P5b]} \\ &= 1 \cdot (x+y) \text{ [P6a]} \\ &= x + y \text{ [P2b]} \end{aligned}$$

3

$$(x+y)(x+y')$$

$$\begin{aligned} &= x + yy' \text{ [P5b]} \\ &= x + 0 \text{ [P6b]} \\ &= x \text{ [P2a]} \end{aligned}$$

4

$$xy + x'z + yz$$

$$\begin{aligned} &= xy + x'z + yz(x+x') \text{ [P6a]} \\ &= xy + x'z + xyz + x'yz \\ &= xy(1+z) + x'z(1+y) \\ &= xy + x'z \text{ [T2a]} \end{aligned}$$

5

$$AB + A'C + BC$$

$$\begin{aligned} &\text{BC is consensus of AB \& A'C} \\ &\text{[T9 Consensus theorem]} \\ &= AB + A'C \end{aligned}$$

6

$$(x+y)(x'+z)(y+z)$$

$$\begin{aligned} &\text{Dual of Ex.4: } AB + A'C + BC \\ &\rightarrow \text{dual is } (A+B)(A'+C)(B+C) \\ &= (A+B)(A'+C) \text{ [Consensus]} \\ &\text{So: } (x+y)(x'+z)(y+z) \\ &= (x+y)(x'+z) \end{aligned}$$

CW 6 — NAND Network: $f(X,Y,Z) = \sum m(0,3,4,5,7)$

Section 4: NAND Implementation (Slide 41 Example)

Mansur Mulk

Given $f(X,Y,Z) = \sum m(0,3,4,5,7)$. (a) Expand to canonical SOP. (b) Simplify using adjacency. (c) Convert to NAND-NAND form and draw.

Step 1

Expand minterms

$$m_0 = X'Y'Z' \quad (000)$$

$$m_3 = X'YZ \quad (011)$$

$$m_4 = XY'Z' \quad (100)$$

$$m_5 = XY'Z \quad (101)$$

$$m_7 = XYZ \quad (111)$$

$$f = X'Y'Z' + X'YZ + XY'Z' + XY'Z + XYZ$$

Step 2

Simplify (adjacency T6)

$$XY'Z' + XY'Z = XY' \quad (z \text{ cancels})$$

$$X'Y'Z' + X'YZ' = Y'Z' \quad (x \text{ cancels})$$

$$X'YZ + XYZ = YZ \quad (x \text{ cancels})$$

$$f = XY' + Y'Z' + YZ$$

Step 3

NAND-NAND form

$$\begin{aligned} f &= XY' + Y'Z' + YZ \\ &= ((XY')' \cdot (Y'Z')' \cdot (YZ)')' \end{aligned}$$

Circuit: Three 2-input NAND gates feeding one 3-input NAND gate

$$= \text{NAND}(\text{NAND}(X,Y'), \text{NAND}(Y',Z'), \text{NAND}(Y,Z))$$

Section 5

Minterms, Maxterms & Canonical Forms

SOM · POM · Example 2.4 · Example 2.5 · Conversions

CW 7 — Identify Minterms & Maxterms

Section 5: Minterms & Maxterms

For each entry: (a) write the minterm m_i and maxterm M_i for the given variable combination; (b) give the complementary relationship.

i	x	y	z	Minterm m_i	Maxterm M_i	Relation
0	0	0	0	$x'y'z'$	$x+y+z$	$(m_0)' = M_0$
3	0	1	1	$x'yz$	$x+y'+z'$	$(m_3)' = M_3$
5	1	0	1	$xy'z$	$x'+y+z'$	$(m_5)' = M_5$
6	1	1	0	xyz'	$x'+y'+z$	$(m_6)' = M_6$
7	1	1	1	xyz	$x'+y'+z'$	$(m_7)' = M_7$
?	0	1	0	? — write it	? — write it	? relation
?	1	0	0	? — write it	? — write it	? relation

✓ Solutions for rows 6 & 7

Row 6: $x=0, y=1, z=0 \rightarrow \text{index} = 010_2 = 2$
 $m_2 = x'yz'$ (0 $\rightarrow$ complement, 1 $\rightarrow$ normal)
 $M_2 = x+y'+z$ (0 $\rightarrow$ normal, 1 $\rightarrow$ complement)
 $(m_2)' = M_2$ ✓

Row 7: $x=1, y=0, z=0 \rightarrow \text{index} = 100_2 = 4$
 $m_4 = xy'z'$
 $M_4 = x'+y+z$
 $(m_4)' = M_4$ ✓

Index rule summary:

Minterm: 1 $\rightarrow$ uncomplemented, 0 $\rightarrow$ complemented

Maxterm: 0 $\rightarrow$ uncomplemented, 1 $\rightarrow$ complemented

CW 8 — Canonical SOM & POM: Examples 2.4 & 2.5 (Mano)

Express each function in both canonical SOM and canonical POM. Show the algebraic expansion and the final index notation.

1 $F(A,B,C) = A + B'C$ (Example 2.4)

→ Express as $\Sigma m(\dots)$ and $\Pi M(\dots)$

✓ Solution — Example 2.4

$$\begin{aligned}\text{Expand: } F &= A(B+B') + B'C \\ &= AB + AB' + B'C \\ &= AB(C+C') + AB'(C+C') + (A+A')B'C \\ &= ABC + ABC' + AB'C + AB'C' + A'B'C\end{aligned}$$

Minterms where $F=1$:

$$A'B'C=m_1, AB'C'=m_4, AB'C=m_5, ABC'=m_6, ABC=m_7$$

$$\therefore F(A,B,C) = \Sigma m(1, 4, 5, 6, 7)$$

POM indices = complement of SOM indices:

$$\{0,1,2,3,4,5,6,7\} \setminus \{1,4,5,6,7\} = \{0,2,3\}$$

$$\therefore F(A,B,C) = \Pi M(0, 2, 3)$$

2 $F(x,y,z) = xy + x'z$ (Example 2.5)

→ Express as $\Pi M(\dots)$ and $\Sigma m(\dots)$

✓ Solution — Example 2.5

$$\begin{aligned}\text{Expand: } F &= xy + x'z = (xy+x')(xy+z) \\ &= (x+x')(y+x')(x+z)(y+z) \\ &= 1 \cdot (x'+y)(x+z)(y+z)\end{aligned}$$

Expand each sum term to 3 variables:

$$(x'+y) = (x'+y+z)(x'+y+z')$$

$$(x+z) = (x+y+z)(x+y'+z)$$

$$(y+z) = (x+y+z)(x'+y+z)$$

Maxterms where $F=0$: M_0, M_2, M_4, M_5

$$\therefore F(x,y,z) = \Pi M(0, 2, 4, 5)$$

SOM indices = complement of POM:

$$\therefore F(x,y,z) = \Sigma m(1, 3, 6, 7)$$

CW 9 — SOM ↔ POM Conversion & Truth Table

Section 5: Canonical Form Conversions

Mansur Mulk

Given $F(x,y,z) = \sum m(2,3,5,7)$. (a) Write the POM form. (b) Complete the truth table. (c) Find $F'(x,y,z)$.

i	x	y	z	F	Minterm/Maxterm
0	0	0	0	0	$M_0 = x+y+z$
1	0	0	1	0	$M_1 = x+y+z'$
2	0	1	0	1	$m_2 = x'yz'$
3	0	1	1	1	$m_3 = x'yz$
4	1	0	0	0	$M_4 = x'+y+z$
5	1	0	1	1	$m_5 = xy'z$
6	1	1	0	0	$M_6 = x'+y'+z$
7	1	1	1	1	$m_7 = xyz$

✓ Answers

(a) POM form:
Maxterm indices = $\{0,1,...,7\} \setminus \{2,3,5,7\} = \{0,1,4,6\}$
 $F(x,y,z) = \prod M(0,1,4,6)$
 $= (x+y+z)(x+y+z')(x'+y+z)(x'+y'+z)$

(b) Truth table: $F=1$ for rows 2,3,5,7 (shaded green)
 $F=0$ for rows 0,1,4,6

(c) Complement F' :
 $F = \sum m(2,3,5,7) \rightarrow F' = \sum m(0,1,4,6)$
OR equivalently: $F' = \prod M(2,3,5,7)$

Key rule: SOM and POM index sets are complementary.
To convert: list the MISSING indices.

Section 6

Standard Forms & Gate Implementation

SOP · POS · NAND-NAND · Circuit Analysis & Synthesis

CW 10 — Circuit Analysis: Majority & XOR-AND Circuit

Derive the Boolean expression for each circuit, simplify, identify the function name, and find the canonical SOM.

1

Circuit 1 — Three AND gates → OR gate (Slide 55)

$$g_1=xy, \quad g_2=yz, \quad g_3=xz; \quad f = g_1 + g_2 + g_3$$

→ Simplify and identify the circuit function.

✓ Solution 1

$$f = xy + yz + xz$$

This is the MAJORITY function:

$F=1$ when at least 2 of the 3 inputs are 1

Truth table check:

$xy+yz+xz = 1$ only for (1,1,0),(1,0,1),(0,1,1),(1,1,1)
i.e., rows 3, 5, 6, 7

Canonical SOM: $\Sigma m(3, 5, 6, 7)$

Canonical POM: $\Pi M(0, 1, 2, 4)$

2

Circuit 2 — XOR-AND circuit (Slide 45 Example)

$$g_1=a \oplus b, \quad g_2=g_1 \cdot c, \quad g_3=ab; \quad f = g_2 + g_3$$

→ Simplify fully and name the function.

✓ Solution 2

$$\begin{aligned} f &= (a \oplus b) \cdot c + ab \\ &= (a'b + ab')c + ab \quad [\text{expand XOR}] \\ &= a'bc + ab'c + ab \quad [\text{distribute}] \\ &= a'bc + a(b'c + b) \quad [\text{factor } a] \\ &= a'bc + a(b+c) \quad [T5: b'c + b = b + c] \\ &= a'bc + ab + ac \end{aligned}$$

$$= ab + ac + bc \quad (\text{MAJORITY function in } a, b, c!)$$

Both circuits implement the same Majority function.

Canonical SOM: $\Sigma m(3, 5, 6, 7)$

Convert each word description into Boolean equations, then express in standard SOP and draw the gate diagram.

1

Burglar Alarm

A = secret switch B = safe in normal position
C = clock (10:00–14:00) D = closet door closed

Alarm triggers if:

- Safe moved with secret switch ON ($A \cdot B'$)
- Closet opened after hours ($D' \cdot C'$)
- Closet opened, switch open ($D' \cdot A'$)

✓ Solution 1

$$\text{Alarm} = AB' + D'C' + D'A'$$

Standard SOP (already minimal):
3 product terms, 6 literals

Gate diagram:

$$\text{NOT}(B) \rightarrow B', \text{NOT}(C) \rightarrow C', \text{NOT}(A) \rightarrow A', \text{NOT}(D) \rightarrow D'$$

$$\text{AND}(A, B') \rightarrow AB'$$

$$\text{AND}(D', C') \rightarrow D'C'$$

$$\text{AND}(D', A') \rightarrow D'A'$$

$$\text{OR}(AB', D'C', D'A') \rightarrow \text{Alarm}$$

$$= 4 \text{ NOT} + 3 \text{ AND} + 1 \text{ OR (standard 2-level SOP)}$$

2

Family Voter Circuit

A=Dad, B=Mom, C=Joe, D=Sue (0=hamburger, 1=chicken)

Rules: (1) Majority vote wins;

(2) If Mom and Dad agree, they override kids;

(3) Otherwise majority of all four wins.

✓ Solution 2

$$F = AB + ACD + BCD$$

Explanation:

$AB \rightarrow$ Mom and Dad both want chicken (override)

$ACD \rightarrow$ Dad + Joe + Sue want chicken (majority)

$BCD \rightarrow$ Mom + Joe + Sue want chicken (majority)

Gate diagram:

$$\text{AND}(A, B) \rightarrow AB$$

$$\text{AND}(A, C, D) \rightarrow ACD$$

$$\text{AND}(B, C, D) \rightarrow BCD$$

$$\text{OR}(AB, ACD, BCD) \rightarrow F$$

$$= 3 \text{ AND} + 1 \text{ OR (clean 2-level SOP)}$$

Quick Reference — Boolean Algebra Classwork Toolkit

CSC 231 · Week 2 · Mansur Mulk

Key Postulates (P1–P6)

P2: $x+0=x$, $x \cdot 1=x$

P3: $x+y=y+x$ (commutative)

P4: $x+(y+z)=(x+y)+z$

P5: $x \cdot (y+z)=xy+xz$

$x+(y \cdot z)=(x+y) \cdot (x+z)$

P6: $x+x'=1$, $x \cdot x'=0$

Key Theorems (T1–T9)

T1: $x+x=x$, $x \cdot x=x$ (idempotent)

T2: $x+1=1$, $x \cdot 0=0$ (null)

T3: $(x')'=x$ (involution)

T5: $x+x'y=x+y$ (simplification)

T6: $AB+AB'=A$ (adjacency)

T8: $(x+y)'=x'y'$ (DeMorgan)

T9: $AB+A'C+BC=AB+A'C$

Canonical Form Rules

SOM: OR of minterms ($F=1$ rows)

POM: AND of maxterms ($F=0$ rows)

Index rule — minterm:

$1 \rightarrow$ uncomplemented, $0 \rightarrow$ complemented

Index rule — maxterm:

$0 \rightarrow$ uncomplemented, $1 \rightarrow$ complemented

$(m_i)' = M_i$ for same index i

Simplification Checklist

1. Adjacency: $AB+AB'=A$
2. Absorption: $A+AB=A$
3. Simplification: $A+A'B=A+B$
4. De Morgan complement
5. Consensus removal:
 $AB+A'C+BC \rightarrow AB+A'C$
6. Distribution/factoring
7. Verify with truth table

SOM $\leftrightarrow$ POM Conversion

$\Sigma m(S) = \Pi M(\text{complement of } S)$

Complement of S : all indices in $\{0, \dots, 2^n-1\}$ NOT in S

Example (3 vars, $n=3$):

$\Sigma m(1,4,7) = \Pi M(0,2,3,5,6)$

F' has same indices, different Σ/Π :

$F=\Sigma m(S) \rightarrow F'=\Sigma m(\text{complement of } S)$

$F=\Sigma m(S) \rightarrow F'=\Pi M(S)$

Gate Implementation

2-level SOP: $\text{AND} \rightarrow \text{OR}$

2-level POS: $\text{OR} \rightarrow \text{AND}$

$\text{NAND-NAND} \equiv \text{AND-OR}$

$\text{NOR-NOR} \equiv \text{OR-AND}$

Building with NAND:

NOT: $A \text{ NAND } A$

AND: NAND then NAND

OR: $\text{NOT}(A) \text{ NAND } \text{NOT}(B)$

Always: 2-level = 2 gate delays